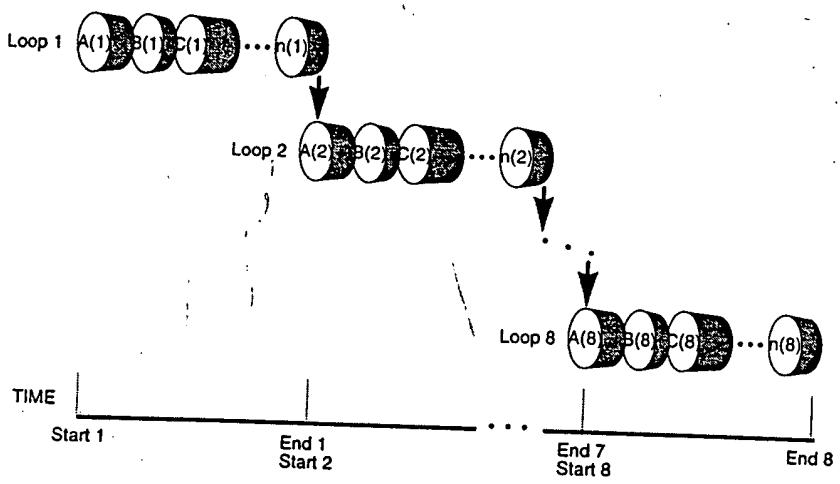
Loop 1
A(1)
B(1)
C(1)
n(1)
Loop 2
A(2)
B(2)
C(2)
n(2)
Loop 8
A(8)
B(8)
C(8)
n(8)
TIME
Start 1
End 1
Start 2
End 7
Start 8
End 8

Figure 1

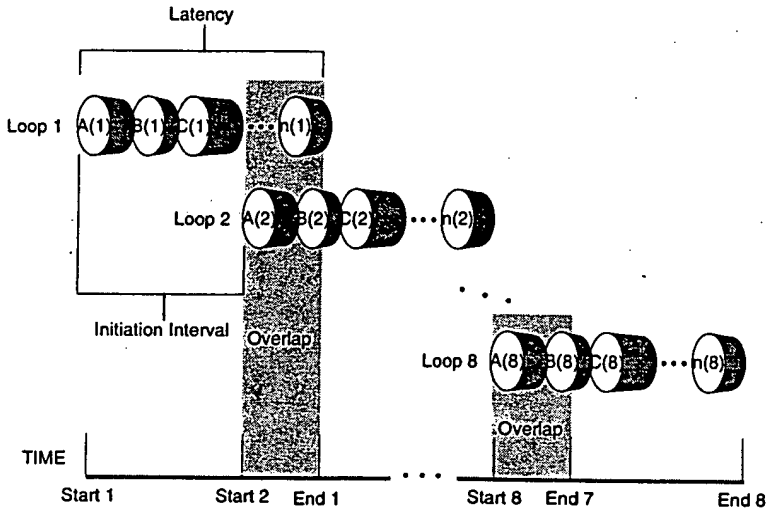
Latency
Loop 1
A(1)
B(1)
C(1)
n(1)
Loop 2
A(2)
B(2)
C(2)
n(2)
Initiation Interval
Overlap
Loop 8
A(8)
B(8)
C(8)
n(8)
Overlap
TIME
Start 1
Start 2
End 1
Start 8
End 7
End 8

Figure 2

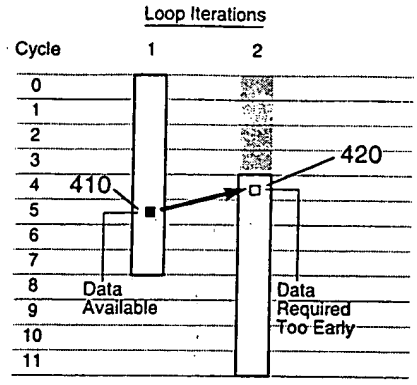

Figure 3 (a)

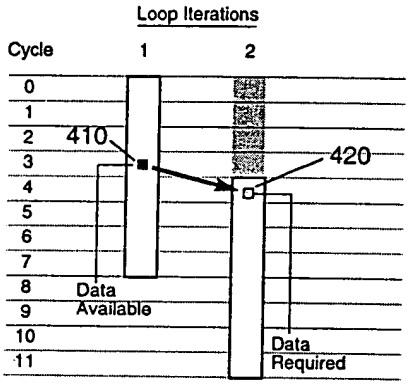

Figure 3 (b)

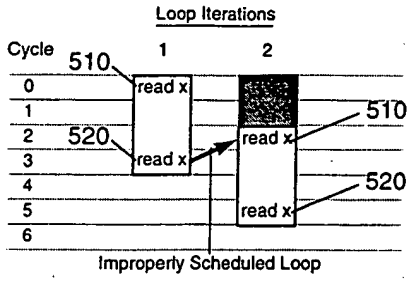

Figure 4 (a)

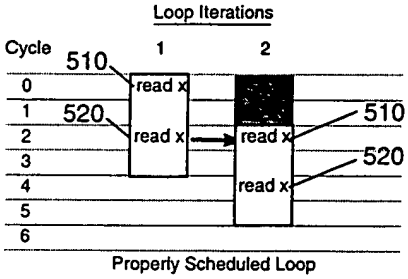

Figure 4 (b)

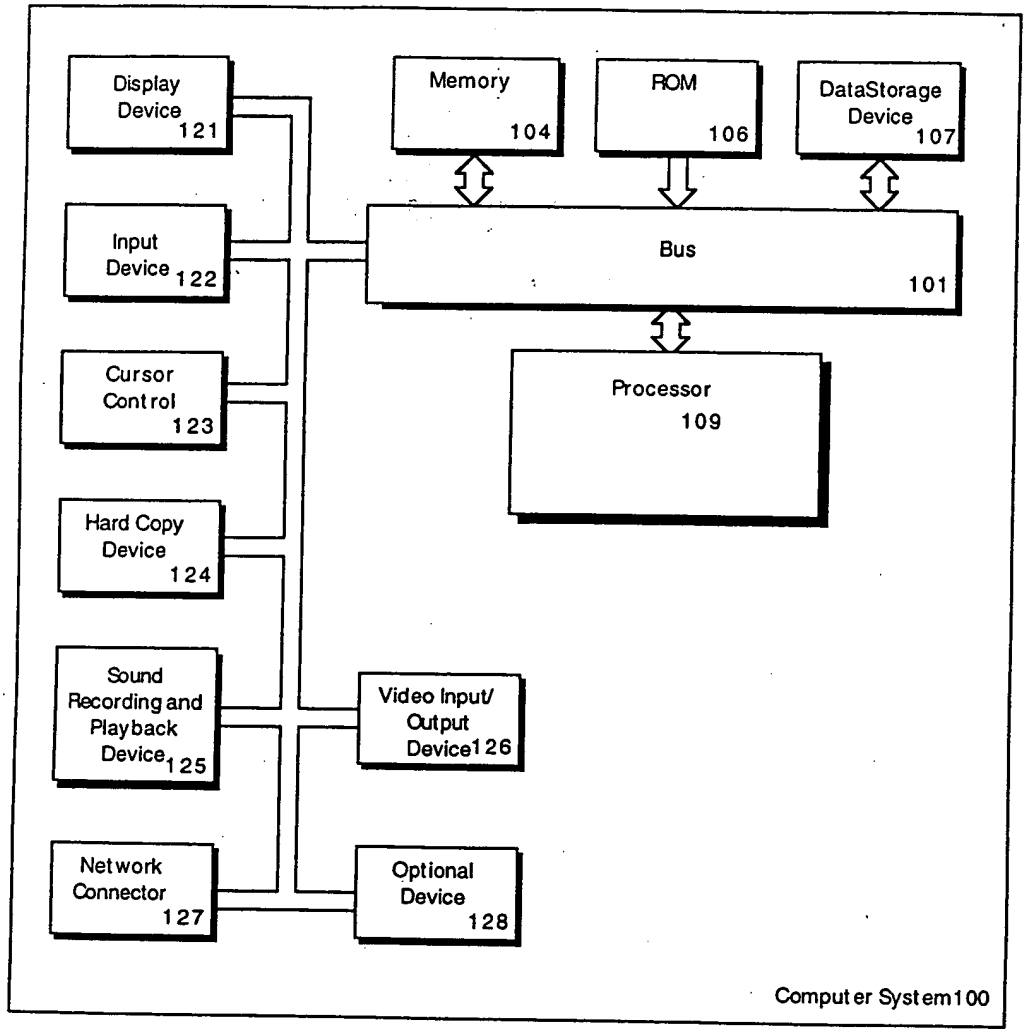
Display Device 121
Memory 104
ROM 106
DataStorage Device 107
Input Device 122
Bus 101
Cursor Control 123
Processor 109
Hard Copy Device 124
Sound Recording and Playback Device 125
Video Input/ Output Device 126
Network Connector 127
Optional Device 128
Computer System 100

Figure 5

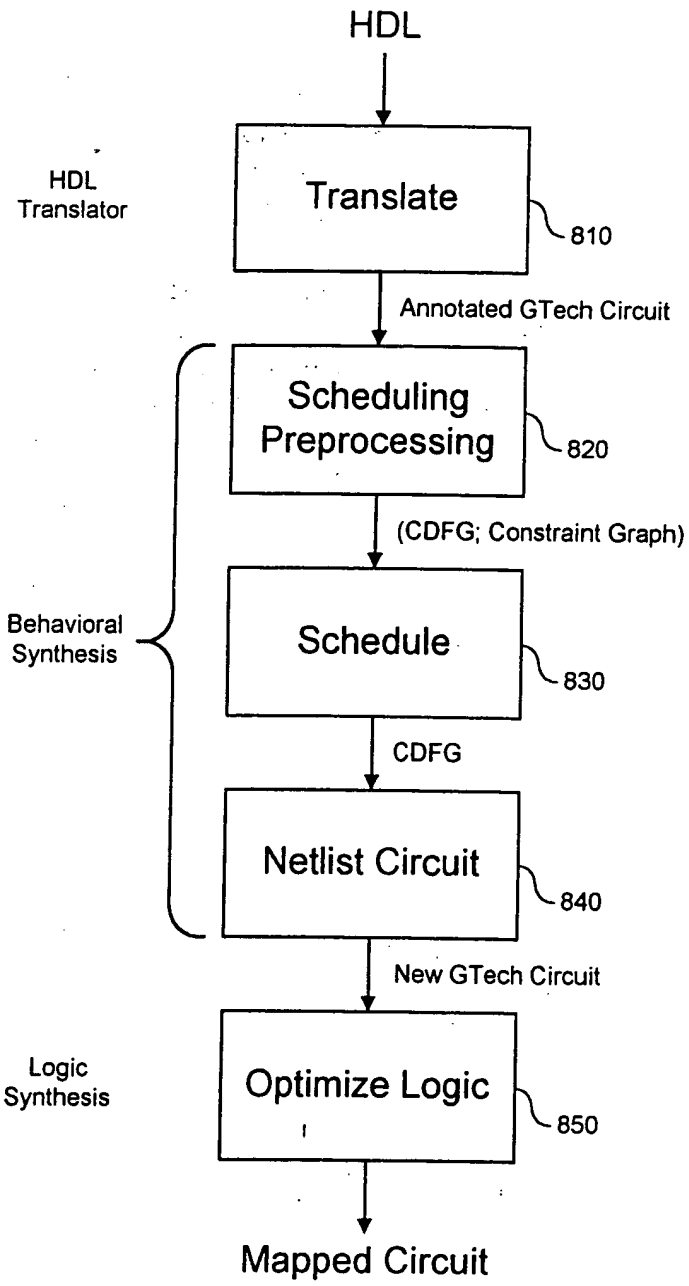

Figure 6 Synthesis with Scheduling

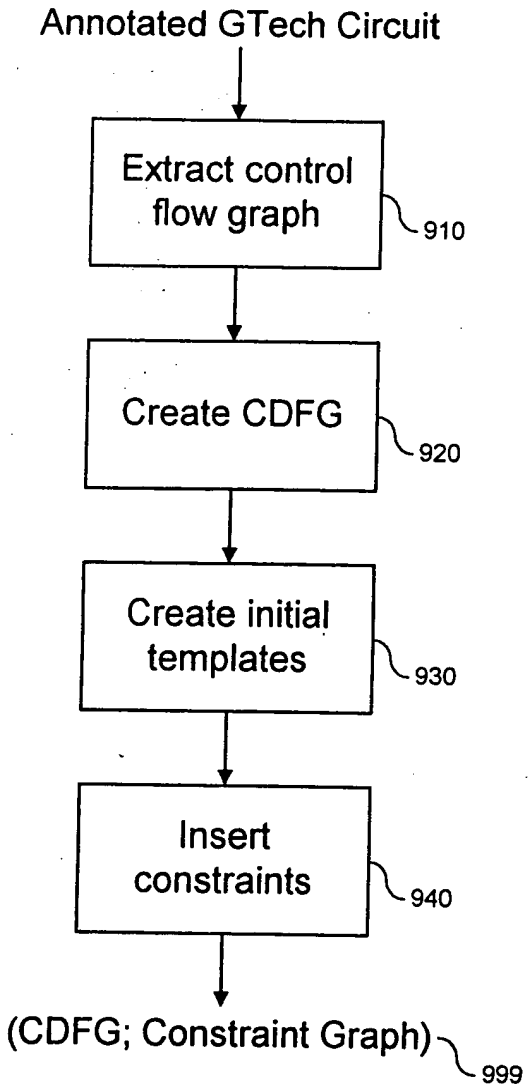

Figure 7

Scheduling Preprocessing

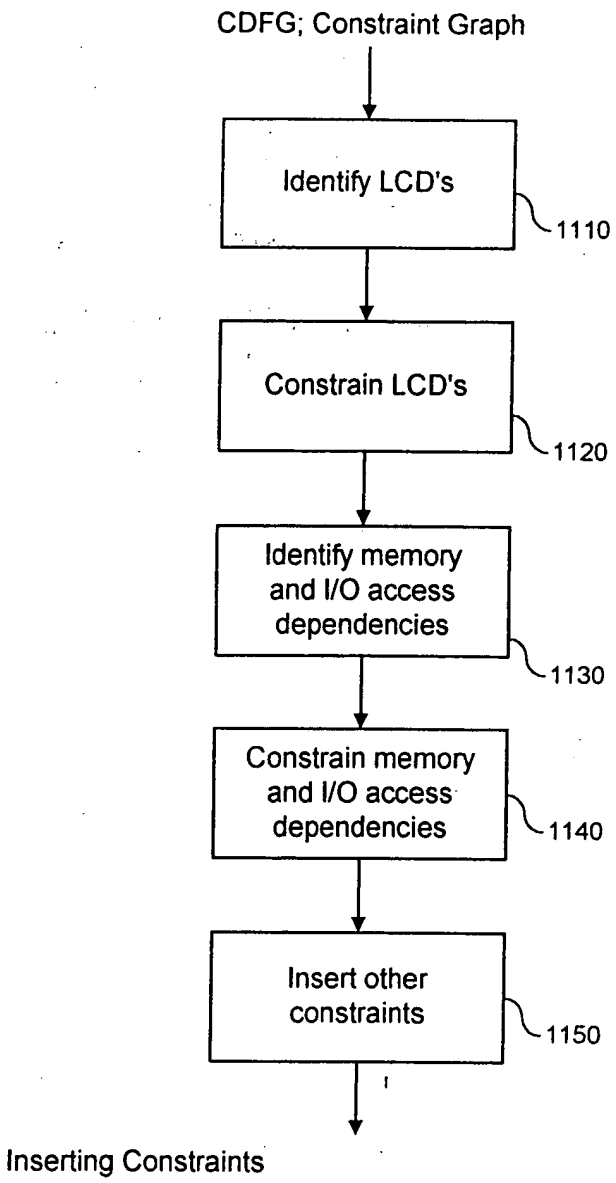
CDFG; Constraint Graph
Identify LCD's
1110
Constrain LCD's
1120
Identify memory and I/O access dependencies
1130
Constrain memory and I/O access dependencies
1140
Insert other constraints
1150
Inserting Constraints

Figure 8

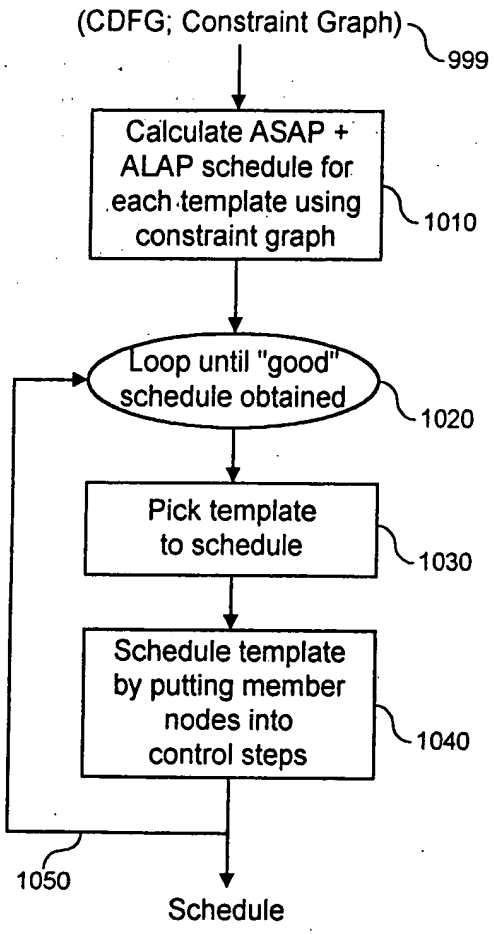

Scheduling Using Templates

Figure 9

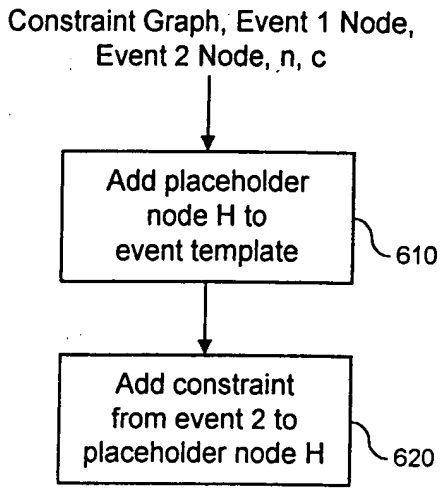
Constraint Graph, Event 1 Node, Event 2 Node, n, c
Add placeholder node H to event template
610
Add constraint from event 2 to placeholder node H
620

Figure 10

```
module loopex8 ( c, x, y, z, clock);
input [1:0] x, y, z;
   input clock ;
   output [2:0] c;
   reg [2:0] c;
   reg [2:0] p;

   always begin                                    3030

        forever begin : theloop                              3010

                c <= x - p ;

                @(posedge clock) ;                          3020

                p = y + z ;

                @(posedge clock) ;

        end

   end

endmodule
```

Figure 11

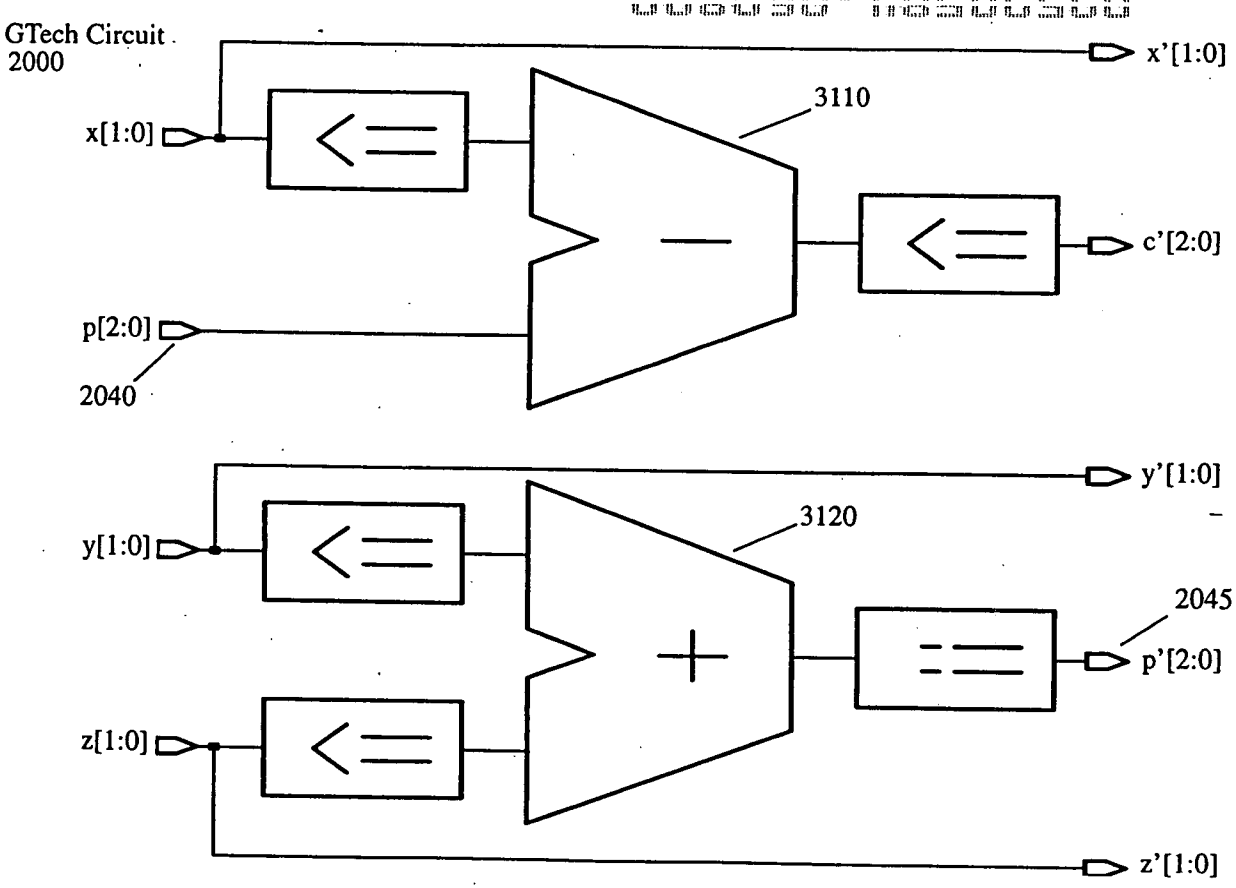
GTech Circuit
2000
x'[1:0]
x[1:0]
3110
c'[2:0]
p[2:0]
2040
y'[1:0]
y[1:0]
3120
2045
p'[2:0]
z[1:0]
z'[1:0]

Figure 12

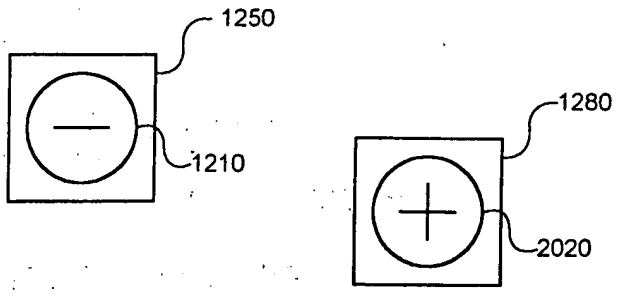

n = 2

Figure 13a

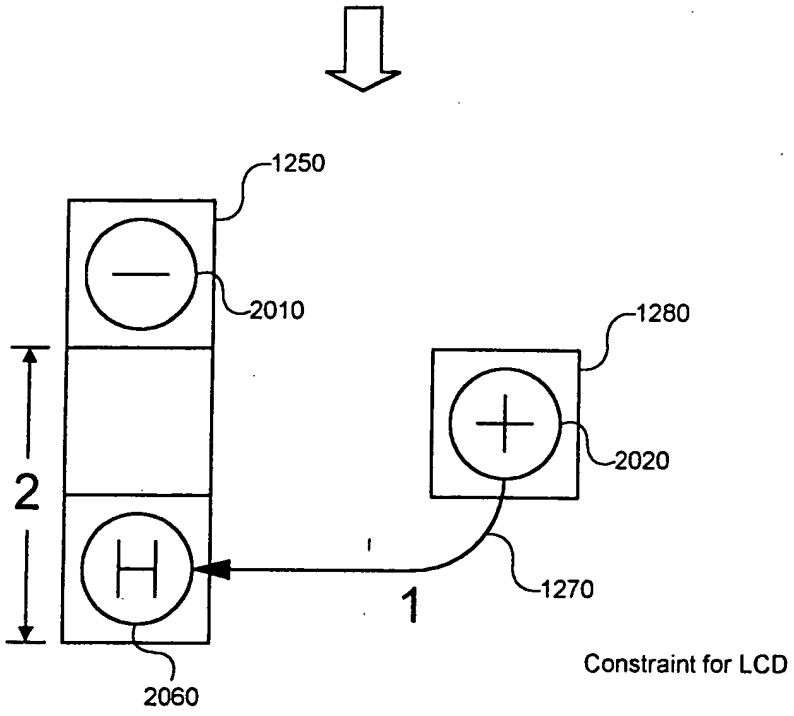

Figure 13b

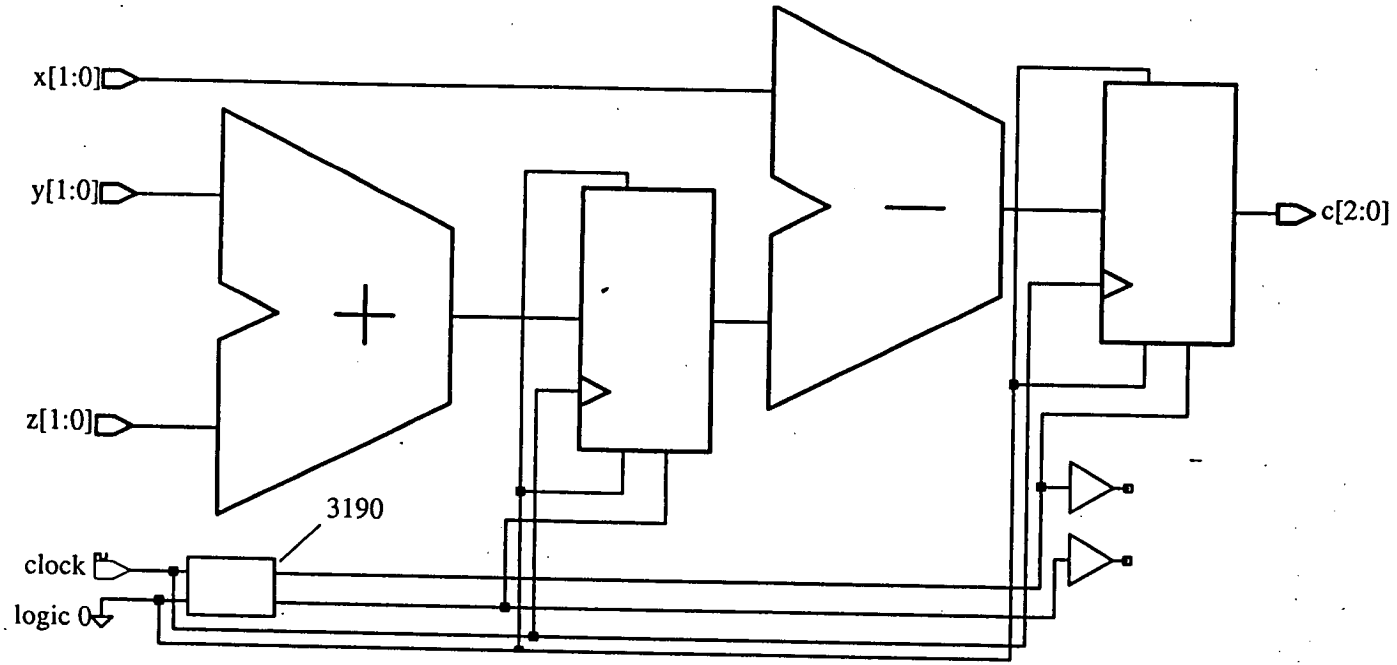

Figure 14

```
module write4 ( w, x, clock);

  input [15:0] x ;
  input clock ;
  output [31:0] w;
  reg [32:0] w;
  reg [15:0] x1 ;
  reg [15:0] x2 ;

  always begin                                    1530

     forever begin : writeloop                    1530

          x1 <= x ;

          @(posedge clock) ;                      1530

          x2 <= x ;

          w <= x1 * x2 ;

     end

  end

endmodule
```

Figure 15

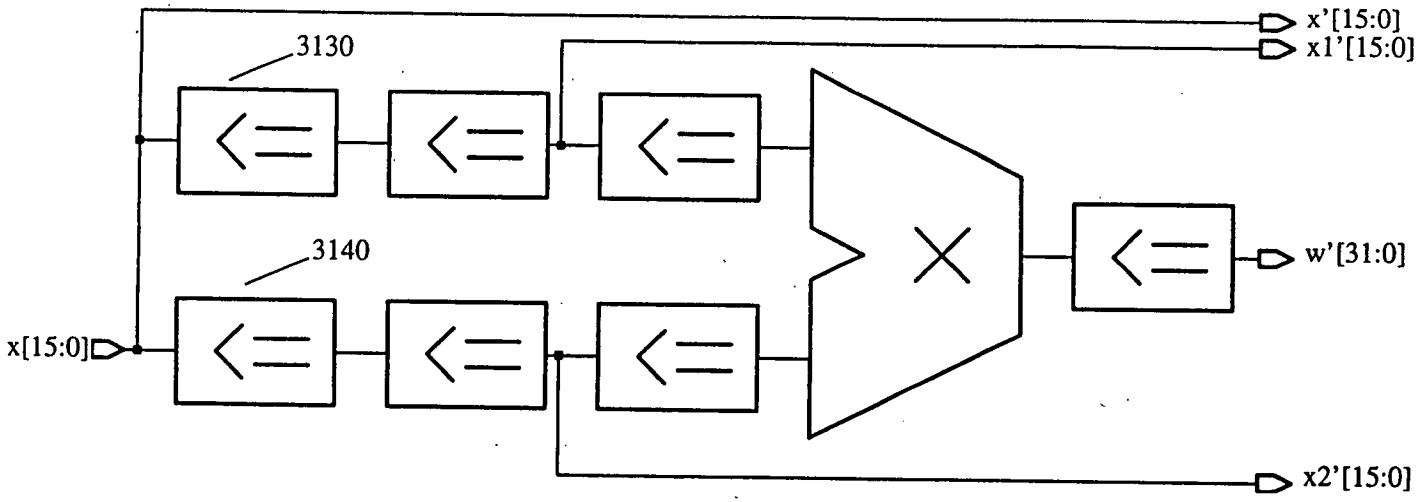

Figure 16

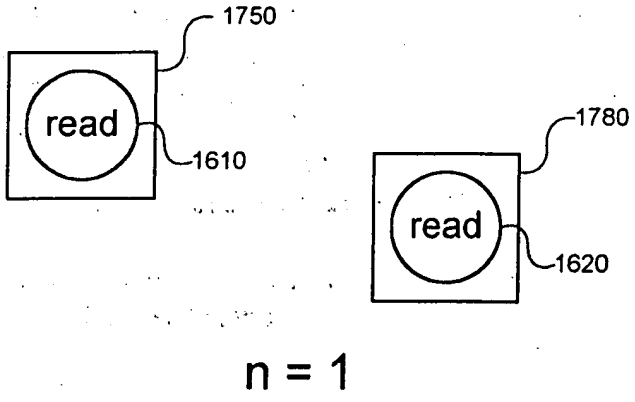

Figure 17a

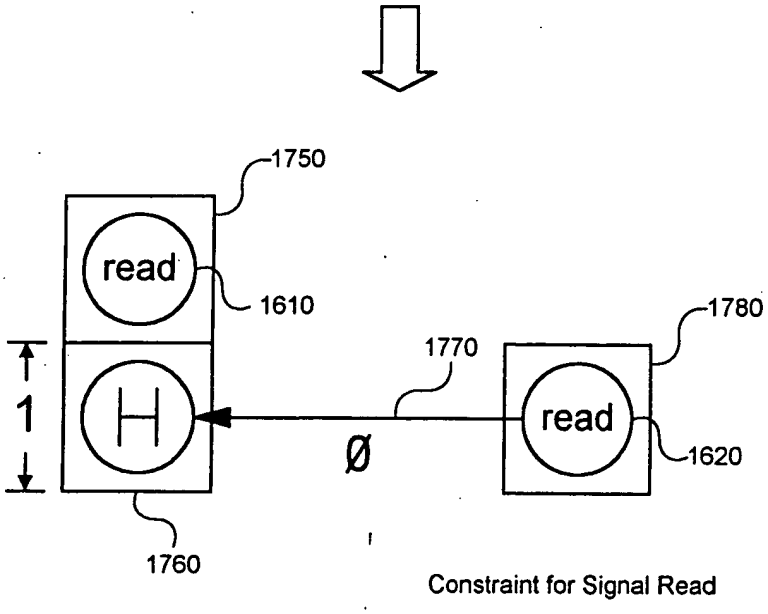

Figure 17b

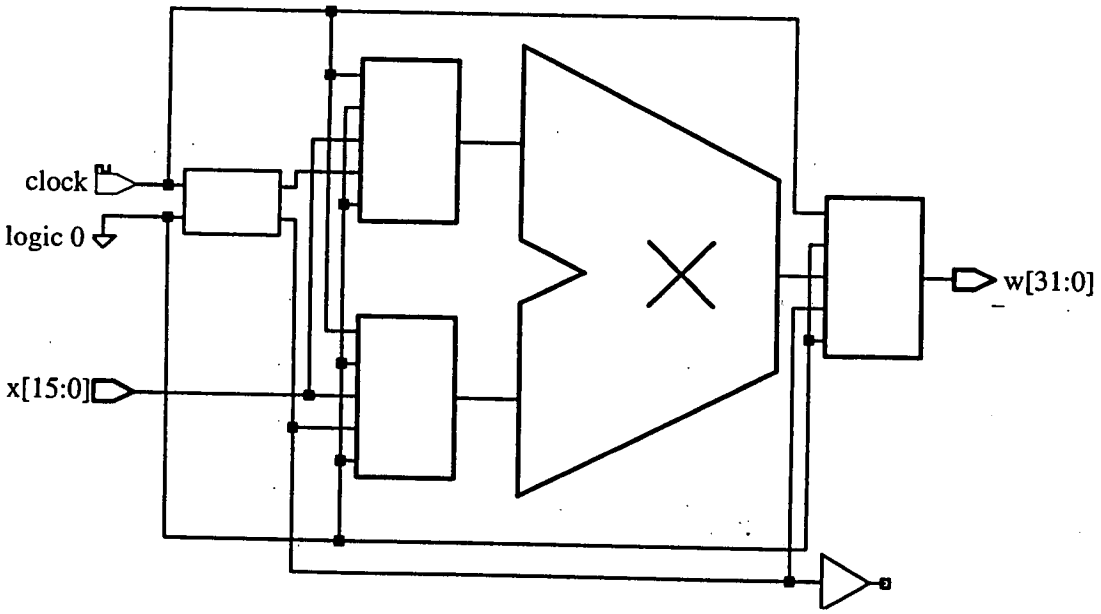

Figure 18

```
module after1 ( c, x, y, z, clock);

  input [1:0] x, y, z;
  input clock ;
  output [2:0] c;
  reg [2:0] c;
  reg [2:0] p;

  always begin

        @(posedge clock) ;

        forever begin
              c <= #24 x - p ;

              @(posedge clock) ;

              p = y + z ;

              @(posedge clock) ;
        end
  end
endmodule
```

Figure 19 (a)

```
entity after1 is
  port(
        c : out integer range 0 to 7;
        x, y, z : in integer range 0 to 3;
        clock : in bit
  );
end after1;

architecture behavioral of after1 is begin
  process
        variable p : integer range 0 to 7;
  begin
        wait until clock'event and clock = '1';

        loop

          c <= transport x - p after 24 ns;

          wait until clock'event and clock = '1';

          p := y + z;

          wait until clock'event and clock = '1';

        end loop;

  end process;
end behavioral;
```

Figure 19 (b)

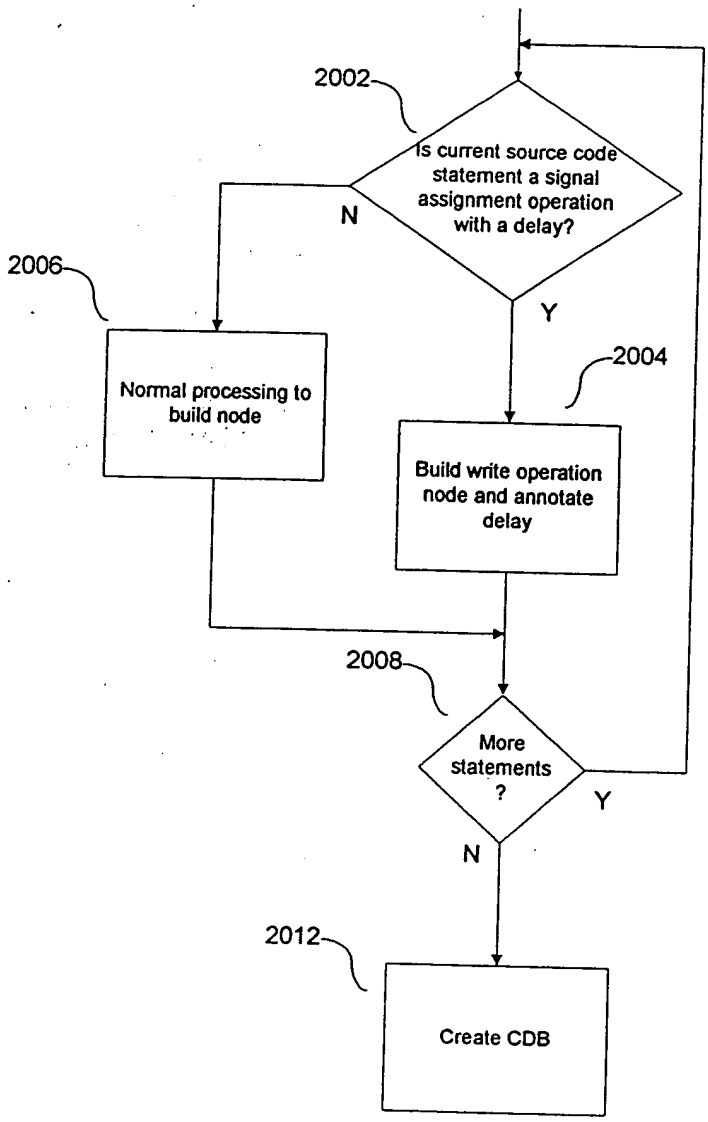
2002
Is current source code statement a signal assignment operation with a delay?
N
Y
2006
Normal processing to build node
2004
Build write operation node and annotate delay
2008
More statements ?
Y
N
2012
Create CDB

Fig. 20

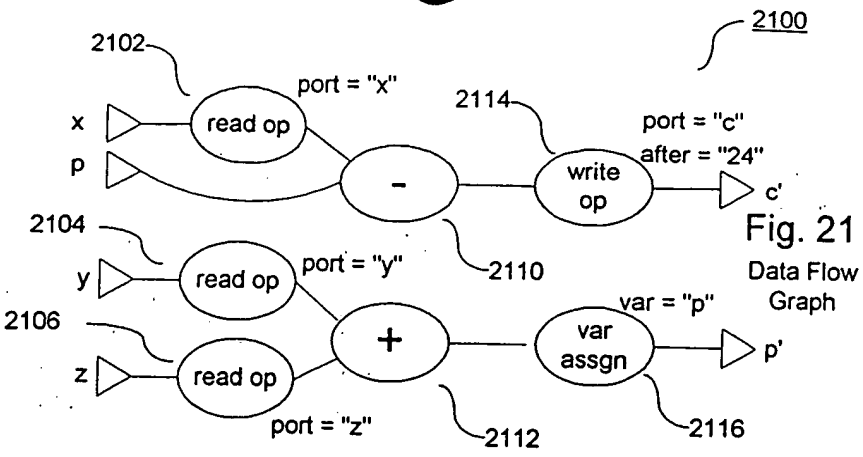

Fig. 21

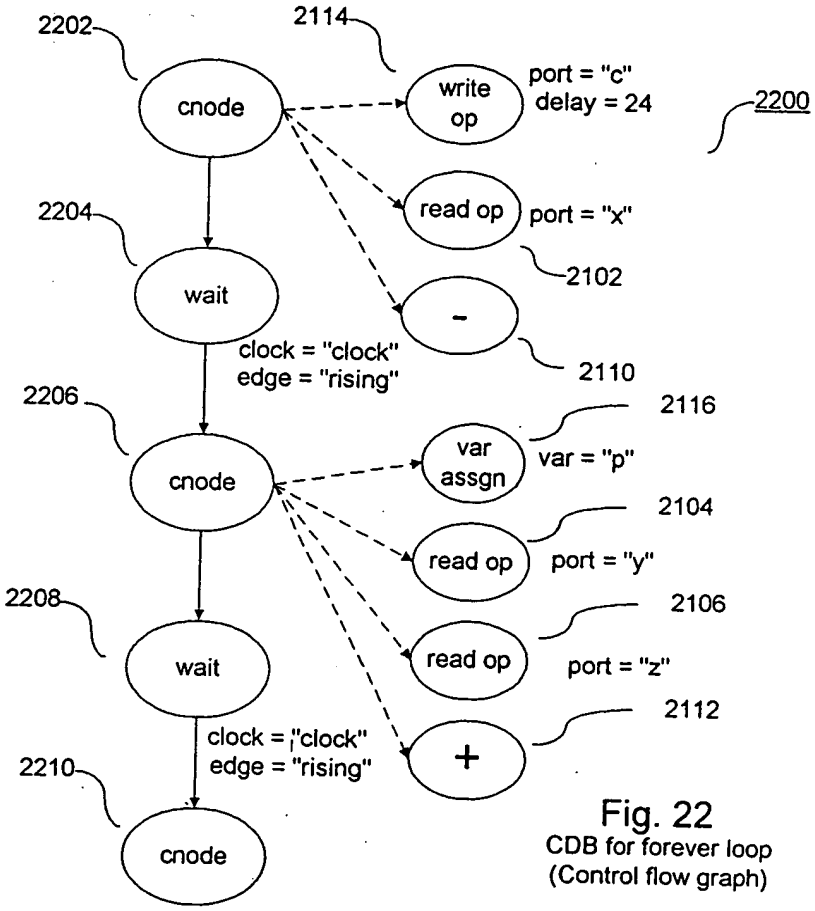

Fig. 22
CDB for forever loop
(Control flow graph)

Fig. 23

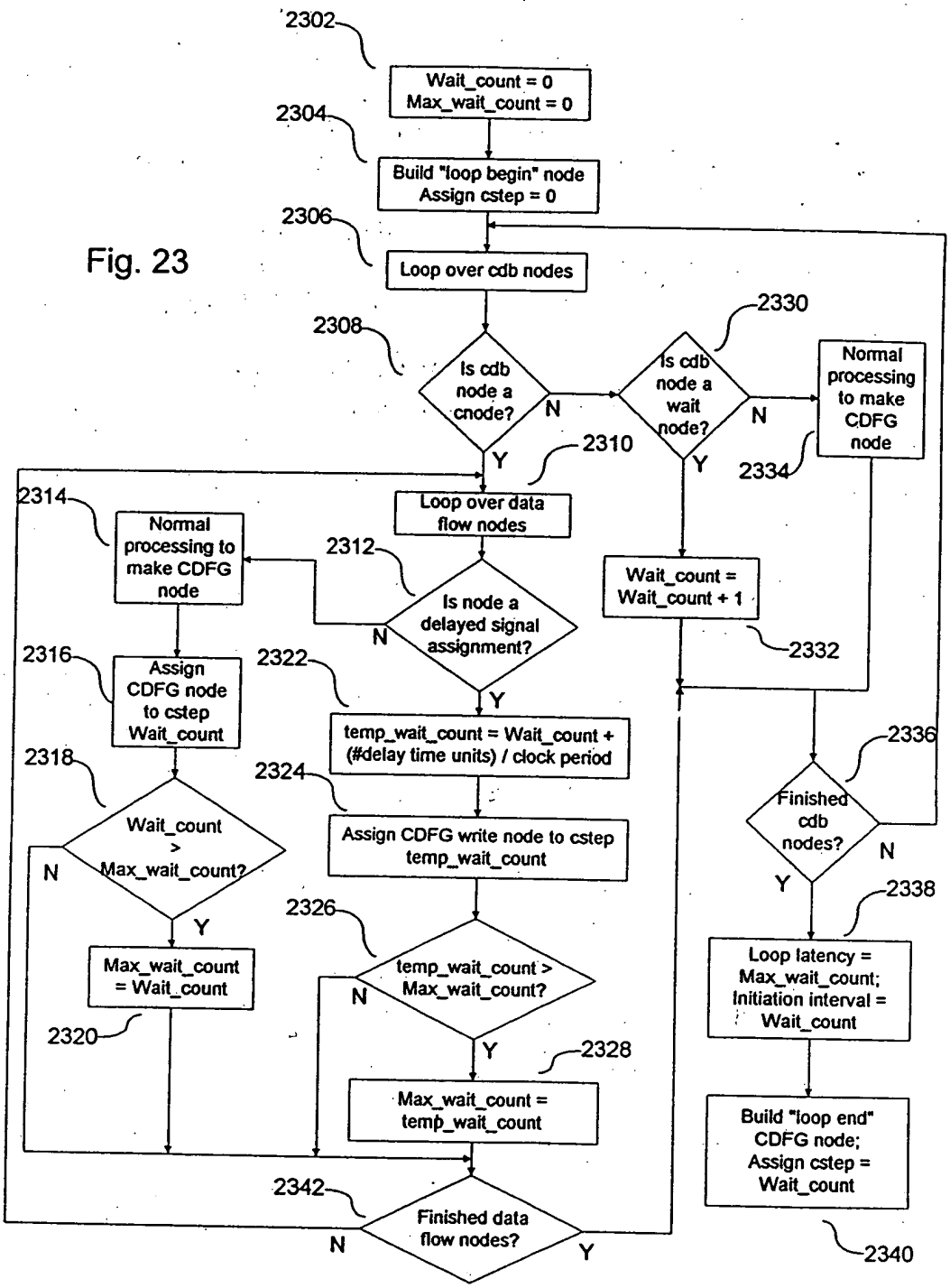
2302
Wait_count = 0
Max_wait_count = 0
2304
Build "loop begin" node
Assign cstep = 0
2306
Loop over cdb nodes
2308
Is cdb node a cnode?
N
Y
2330
Is cdb node a wait node?
N
Y
Normal processing to make CDFG node
2334
2310
Loop over data flow nodes
2314
Normal processing to make CDFG node
2312
Is node a delayed signal assignment?
N
Y
Wait_count = Wait_count + 1
2332
2316
Assign CDFG node to cstep Wait_count
2322
temp_wait_count = Wait_count + (#delay time units) / clock period
2318
Wait_count > Max_wait_count?
N
Y
2324
Assign CDFG write node to cstep temp_wait_count
2326
temp_wait_count > Max_wait_count?
N
Y
Max_wait_count = Wait_count
2320
2328
Max_wait_count = temp_wait_count
2342
Finished data flow nodes?
N
Y
2336
Finished cdb nodes?
N
Y
2338
Loop latency = Max_wait_count; Initiation interval = Wait_count
Build "loop end" CDFG node; Assign cstep = Wait_count
2340

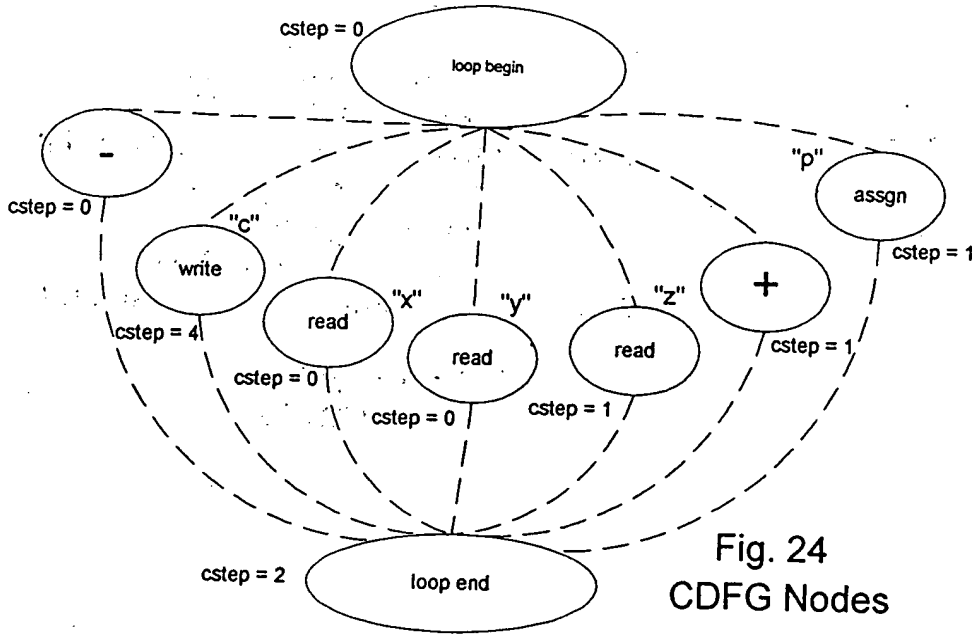

Fig. 24
CDFG Nodes

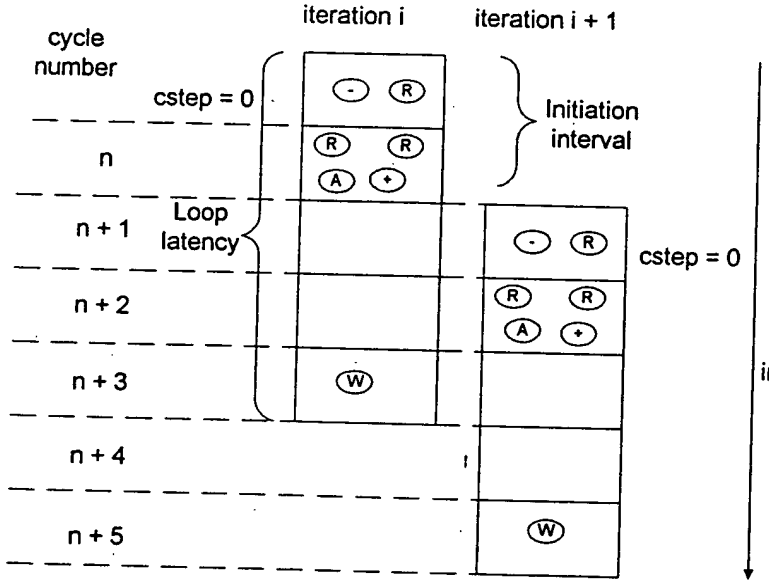

Fig. 26

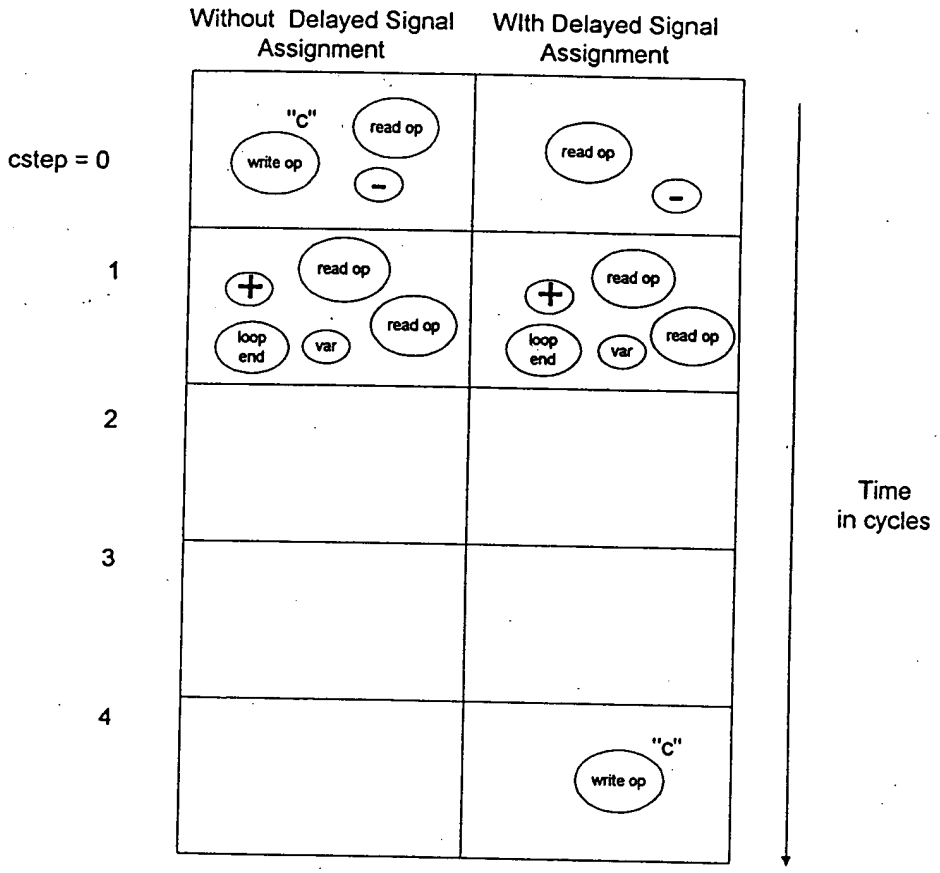
Without Delayed Signal Assignment
With Delayed Signal Assignment
cstep = 0
1
2
3
4
"c"
write op
read op
read op
loop end
var
read op
read op
loop end
var
read op
"c"
write op
Time in cycles

Fig. 25

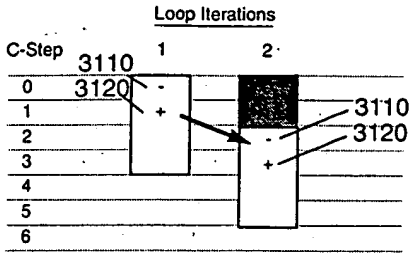

Figure 27

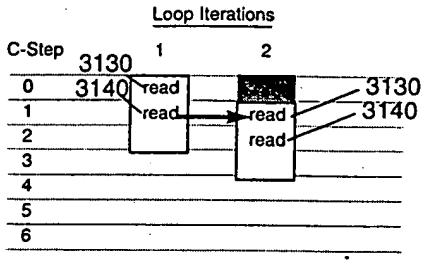
Loop Iterations
C-Step
1
2
3130
3140
read
read
read
read
3130
3140
0
1
2
3
4
5
6

Figure 28